

南華大學九十五學年度學士班暨進修學士班
轉學生招生考試考試試題卷

招生
學系

學士班 3 年級資訊工程學系

編號：D2-28-26

科目：電子學

試題紙第 / 頁共 / 頁

- Terminologies explanation: (15 points)
(a) LED (b) IC (c) nanometer (d) OPA (e) MOS
- As shown in Fig. 1, given a LED with the forward bias of 1.5V and the forward current range of 15-25 mA, if the DC 36V is added on the LED and calculate the reasonable range of the series resistance R. (14 points)

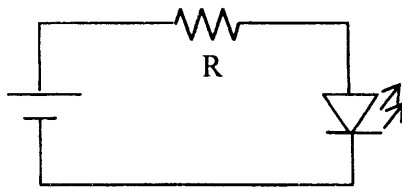


Fig. 1 A LED display

- A clipper (截波器) is shown in Fig. 2, if the input V_i is a sine waveform of $\pm 20V$ and the reference voltage of E is 4V, show the waveform of output voltage V_o . (14 points)

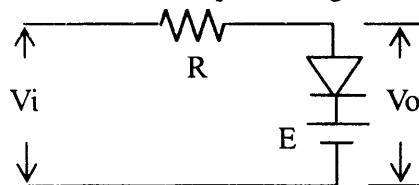


Fig. 2 A clipper

- A clamper (箝位器) is shown in Fig. 3, if the input V_i is a sine waveform of $\pm 20V$ and show the waveform of output voltage V_o . (14 points)

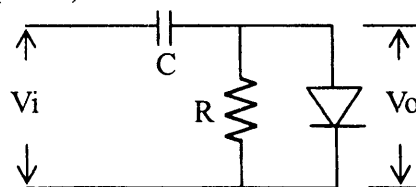


Fig. 3 A clamper

- What the major differences are for CE, CC, and CB amplifiers in terms of A_v , input impedance, and output impedance. (14 points)

	A_v (Voltage gain)	input impedance	output impedance
CE			
CC			
CB			

- Show the equivalence of different numerical systems. (16 points)
 $41.375_{(10)} = \underline{\hspace{2cm}}_{(2)} = \underline{\hspace{2cm}}_{(8)} = \underline{\hspace{2cm}}_{(16)} = \underline{\hspace{2cm}}_{(BCD)}$

- An OPA adder is shown in Fig. 4, if $V_1 = 2V$, $V_2 = 1.5V$, and $V_3 = -0.5V$, then find the output voltage V_o . (13 points)

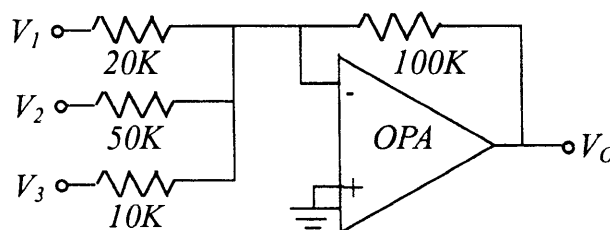


Fig. 4 An OPA adder